

HW #3
CSc 137, Harvey
Adder/Mux (12 pts)

1. Design a Single cell -1 bit Carry propagate (Ripple Carry Adder) full adder. (6 pts)
 - a. Generate the truth table
 - b. Using K-map, determine the logical expression for Carry out (C-out) and Sum (S)
 - c. Based on the logical expression, create the schematic diagram for full adder
2. Design a 1 bit, 2 to 1 multiplexer (Mux). Outputs Y when S = 0; X when S = 1. (6 pts)
 - a. Generate the truth table
 - b. Using K-map, determine the logical expression for output
 - c. Based on the logical expression, create the schematic diagram for Mux

①. Design a single cell -1 bit Carry Propagate (Ripple Carry Adder) full adder.

a) Generate Truth Table

	Inputs			Outputs	
	A_x	B_x	C_{in}	$S_{sum\ output}$	C_{out}
R1	0	0	0	0	0
R2	0	0	1	1	0
R3	0	1	0	1	0
R4	0	1	1	0	1
R5	1	0	0	1	0
R6	1	0	1	0	1
R7	1	1	0	0	1
R8	1	1	1	1	1

b) Using K-map, determine the logical expression for Carry out (C-out) and Sum (S)

$$S = R_2 + R_3 + R_5 + R_8$$

$$C_{out} = R_4, R_6, R_7, R_8$$

$$S = \bar{A}_x \bar{B}_x C_x + \bar{A}_x B_x \bar{C}_x + A_x \bar{B}_x \bar{C}_x + A_x B_x C_x$$

$$= A \oplus B \oplus C$$

$$C_{out} = \bar{A}_x B_x C_x + A_x \bar{B}_x C_x + A_x B_x \bar{C}_x + A_x B_x C_x$$

$$= A_x C_x + B_x C_x + A_x B_x$$

S K-map:

A_x	$B_x C_x$			
	00	01	11	10
0		1		1
1	1		1	

imp 1 imp 2

$$S = \bar{B}_x + B_x$$

$$= A_x \oplus B_x \oplus C_x$$

Cout K-map:


		$B \times C_x$			
A_x		00	01	11	10
0				1	
1			1	1	1

imp 1 imp 2 imp 3

$$Cout = A_x C_x + B_x C_x + A_x B_x$$

c) Based on the logical expression,
create the schematic diagram for full adder

A_x B_x C_x

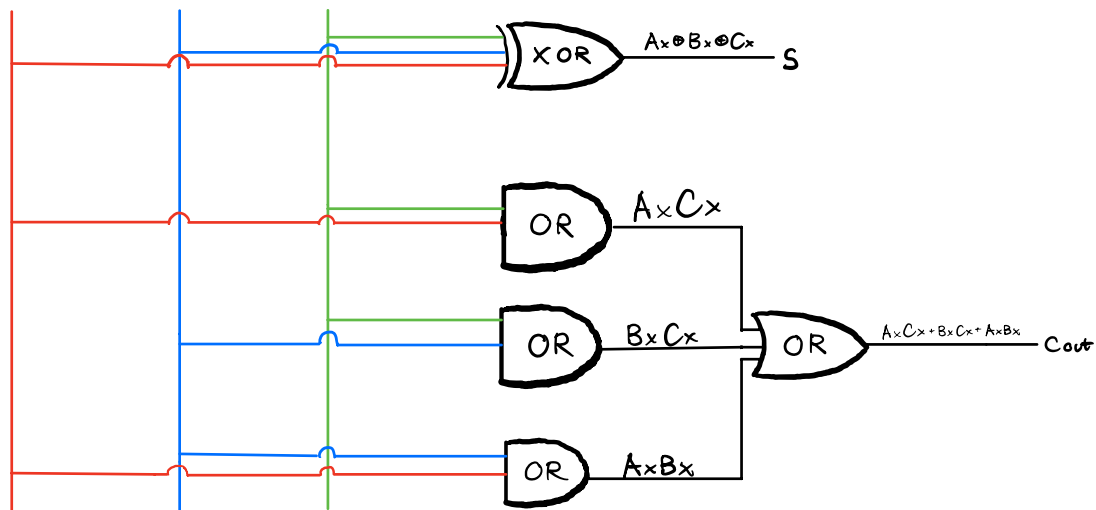

② Design a 1-bit, 2 to 1 MUX.

Output Y when $S=0$, X when $S=1$

a) Generate truth table

control signal	input signals		output
S	x	y	r
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Y when $S=0$

X when $S=1$

b) Using K-Map, determine the logical expression for output

when $r=1$: $r = \underbrace{\bar{S}\bar{x}y}_{R2}, \underbrace{\bar{S}xy}_{R4}, \underbrace{Sx\bar{y}}_{R7}, \underbrace{Sxy}_{R8}$

$S \backslash xy$	$C1$	$C2$	$C3$	$C4$
S	00	01	11	10
$R1$ 0		1	1	
$R2$ 1			1	1

implicant 1 imp 2 imp 3

$$r = \begin{matrix} 001 \\ 011 \end{matrix} + \begin{matrix} 011 \\ 111 \end{matrix} + \begin{matrix} 111 \\ 110 \end{matrix} = \bar{S}y + \cancel{xy} + sx = \bar{S}y + sx$$

c) Based on the logical expression,
create the schematic diagram for MUX
 $r = \bar{s}y + sx$

