

Kevin Cendana

HW#6

CSc 137, Singh

(20 Points)

For problems 6.1 through 6.3: Suppose the propagation delay of an 8-bit adder is 0.8ns, adder/subtractor is 1.1ns, 2-to-1 mux is 0.3ns, and 4-to-1 mux is 0.6ns. Also, assume register setup time (τ_{st}), clock-to-q (τ_{cq}), and clock-skew (τ_{cs}) are all 0.05ns. (15 points)

6.1 Calculate the required maximum clock frequency for each of the following data paths:

a. Single-cycle data path in Fig. 6.2.

$$\tau \geq 2\Delta_{ADD} + \Delta_{ADD/SUB} + \tau_{st} + \tau_{cq} + \tau_{cs}$$

① delay in ns: $0.8 + 0.8_{ns} + 1.1_{ns} + 0.05_{ns}(3) = 2.85_{ns}$
 in ns' adder adder adder/subtractor $\tau_{st} + \tau_{cs} + \tau_{cq}$

② ns $\rightarrow \mu s$: $2.8_{ns} \cdot \frac{10^{-3}ms}{1ns} = 0.028\mu s$

③ time \rightarrow frequency (μs)
 $\frac{1}{period} = \frac{1}{0.0028\mu s} = \sim 357_{mhz}$

b. Multi-cycle data path in Fig. 6.3.

① delay in ns:

$$\tau \geq \Delta_{MUX1} + \Delta_{ADD/SUB} + \Delta_{MUX2} + \tau_{st} + \tau_{cq} + \tau_{cs}$$

$0.3 + 1.1 + 0.6 + 0.05(3) = 2.15_{ns}$
 mux1 add sub mux2 $\tau_{st} + \tau_{cs} + \tau_{cq}$

② ns $\rightarrow \mu$: $2.15_{ns} \cdot \frac{10^{-3}\mu s}{1ns} = 0.00215\mu s$

③ time \rightarrow Freq
 $\frac{1}{period(\mu s)} = \frac{1}{0.00215} = \sim 465_{mhz}$

c. Pipelined data path in Fig. 6.4.

① $4 \cdot 0.15 + (4-1) \cdot 0.15 + 3 \cdot 0.15 + 0.8(2) + 1.1 = 4.2_{ns}$

② ns $\rightarrow \mu$: $4.2_{ns} \cdot \frac{10^{-3}\mu s}{1ns} = 0.0042\mu s$

③ time \rightarrow freq: $\frac{1}{0.0042\mu s} = 238_{mhz}$

6.2 Estimate the speedup between the following data paths when generating $N = 1000$ quantities $A_i + B_i + C_i \pm D_i$ for $i = 0, 1, 2, \dots, 999$. Ignore the data reading and writing delays. (5 points)


a. Problem 6.1a vs. 6.1c

$$Speed\ up = \frac{NF}{K+N-1} = \frac{(1000)(3)}{3+1000-1} = \frac{3000}{1002} = 2.99$$

Extra Credit: 10 points

 - 5.1 Non-return-to-zero inverted (NRZI) is a data coding scheme used to communicate with USB devices. The output signal (z) of a NRZI generator transitions when the input bit (x) is 0 and remains at constant previous value (0 or 1) when the input bit is 1. That is, from right to left when the input to the NRZI generator is 0 0 0 0 0, its output from right to left will transition as 1 0 1 0 1 0. Its output for consecutive 1s at the input, however, will remain at the previous output value. For example, the NRZI generator outputs from right to left z : 0 0 0 0 0 1 0 1 1 1 0 1 0 1 1 for input X : 1 1 1 1 0 0 0 1 1 1 0 0 0 0 1 1 read from right to left. Likewise, for $X = 0xCF0C$, Z : $0xEFAE$. Design the NRZI generator. Design the circuit for the NRZI (Hint: design a Mealy FSM). (5 points)

ex) $1 \rightarrow r$
 corr: 1 1 1 0 1 0 1 1 1 0 1 0 0 0 0
 in: 1 1 0 0 0 0 1 1 1 0 0 0 1 1 1
 out: 1 1 0 1 0 1 1 1 0 1 0 0 0 0 0



current state	input	next	output
q_0	x	d_0	z
0	0	1	1
0	1	0	0
1	0	0	0
1	1	1	1

$$d_0 = z + \bar{q}_0 \bar{x} + q_0 x$$

$$x \text{ AND } q_0 \text{ OR } \bar{x} \text{ AND } \bar{q}_0 \text{ OR } z$$

$$= x \text{ XNOR } q_0 \text{ OR } z$$

